 


Preparação Teste

- Flip flop
- Registrador
- Contador
- **Maquina com contador em memória**
- **Maquina com porta**
- **Maquina em memória para controle (elevador)**
- **Maquina para memória cache**


Máquina com Contador

Contador para sequencia 0,2,0,3,0,2,0,3...
solução 4 estados




Máquina com Contador

 Contador para sequencia 0,2,0,3,0,2,0,3...
solução 4 estados



0 =	00	tudo desligado
2 =	10	liga motor sobe
0 =	00	desliga
3 =	11	liga motor e desce

Máquina com Contador

 

Estado

0

1

2

3

Proximo Saida

1

0

2

2

3

0

0

3

Máquina com Contador

Estado

Proximo Saida

0	1=01	0=00
1	2=10	2=10
2	3=11	0=00
3	0=00	3=11

4 bits

2 bits para proximo


2 bits para saida

Estado

Proximo Saida

0	01	00 =4
1	10	10 =A
2	11	00 =C
3	00	11 =3

Máquina com Contador

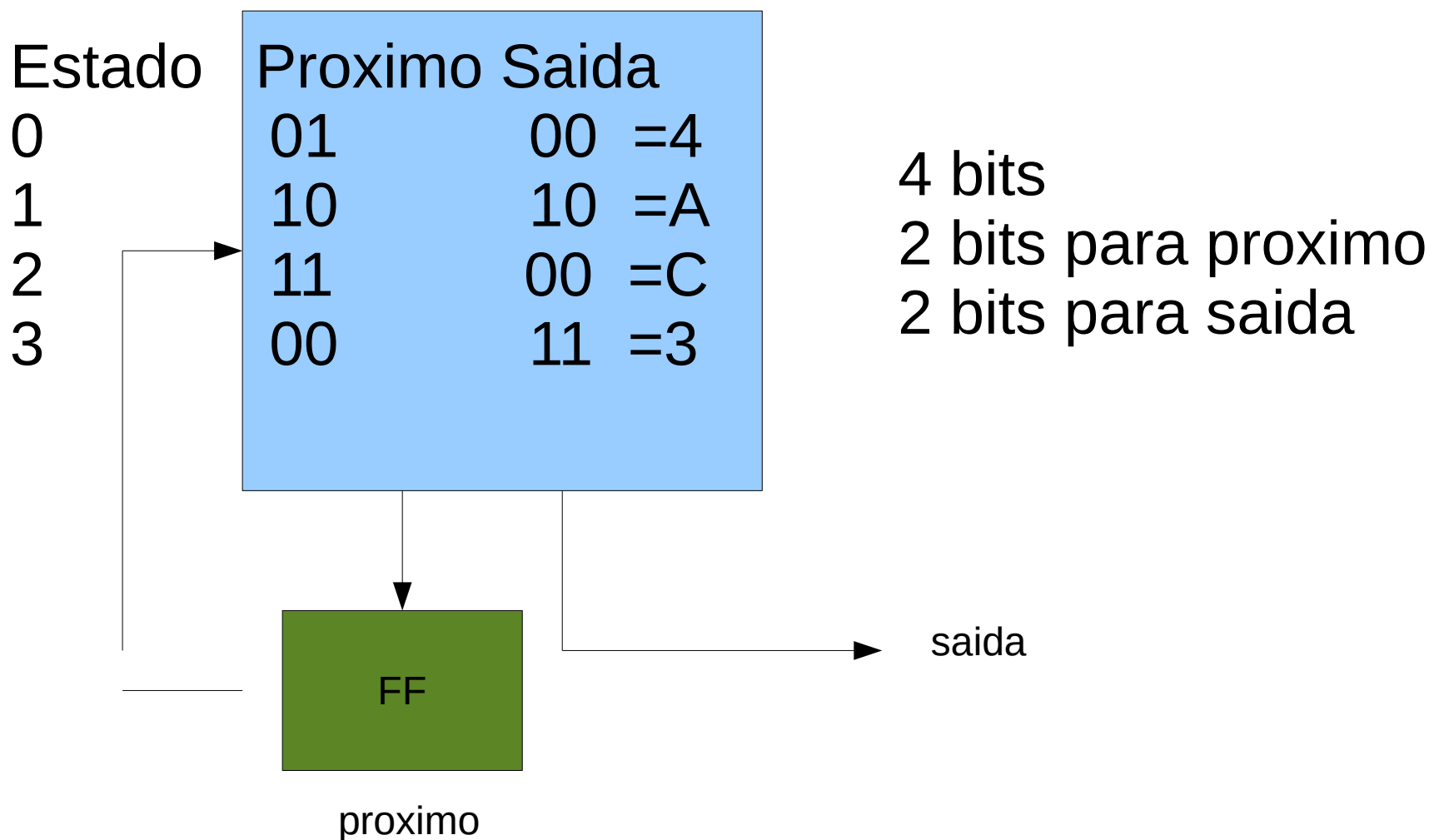

ROM em VHDL

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.Numeric_Std.all;

entity rom_contador1 is
  port (address : in std_logic_vector (1 downto 0);
        data : out std_logic_vector (3 downto 0));
end entity rom_contador1;

architecture fsmrom of rom_contador1 is
  type rom_array is array (0 to 3) of std_logic_vector(3 downto 0);
  constant rom : rom_array := ("0100",
                                "1010",
                                "1100",
                                "0011"
                                );
begin
  data <= rom(to_integer(unsigned(address)));
end architecture fsmrom;
```

Usando a ROM com FSM

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
library work;  
use work.ALL;  
use IEEE.Numeric_Std.all;
```

```
entity fsm_contador1 is  
port ( clk : in std_logic;  
       count : out std_logic_vector(1 downto 0));  
end fsm_contador1;
```


```
architecture Behavioral of fsm_contador1 is  
signal address : std_logic_vector(1 downto 0);  
signal data : std_logic_vector(3 downto 0);  
begin  
rom : entity work.rom_contador1 port map(address,data);
```

```
fsmMemory : process(clk)  
begin
```

```
    if (clk = '1' and clk'event) then  
        address <= data(3 downto 2);  
        count <= data(1 downto 0);  
    end if;
```

```
end process;
```


```
end Behavioral;
```

 

Síncrono para a Máquina
De estados funcionar....

Com Sinais de Entrada

 - Contador com uma entrada A
- Se $A=0$, contar 0,1,2,3,0,1,2,3,.....
- Se $A=1$, contar 3,2,1,0,3,2,1,0,....



Com Sinais de Entrada


 


Tabela ???

4 estados, 1 entrada, 2 bits de saída

Com Sinais de Entrada

 


A	Estado
0	00
0	01
0	10
0	11
1	00

.....

Proximo	Saida
01	0
10	1
11	2
00	3
11	3

Com Sinais de Entrada

 


Estado	A
00	0
00	1
01	0
01	1
10	

.....

Proximo	Saida
01	0
11	3
10	1
00	0

Circuito com entrada

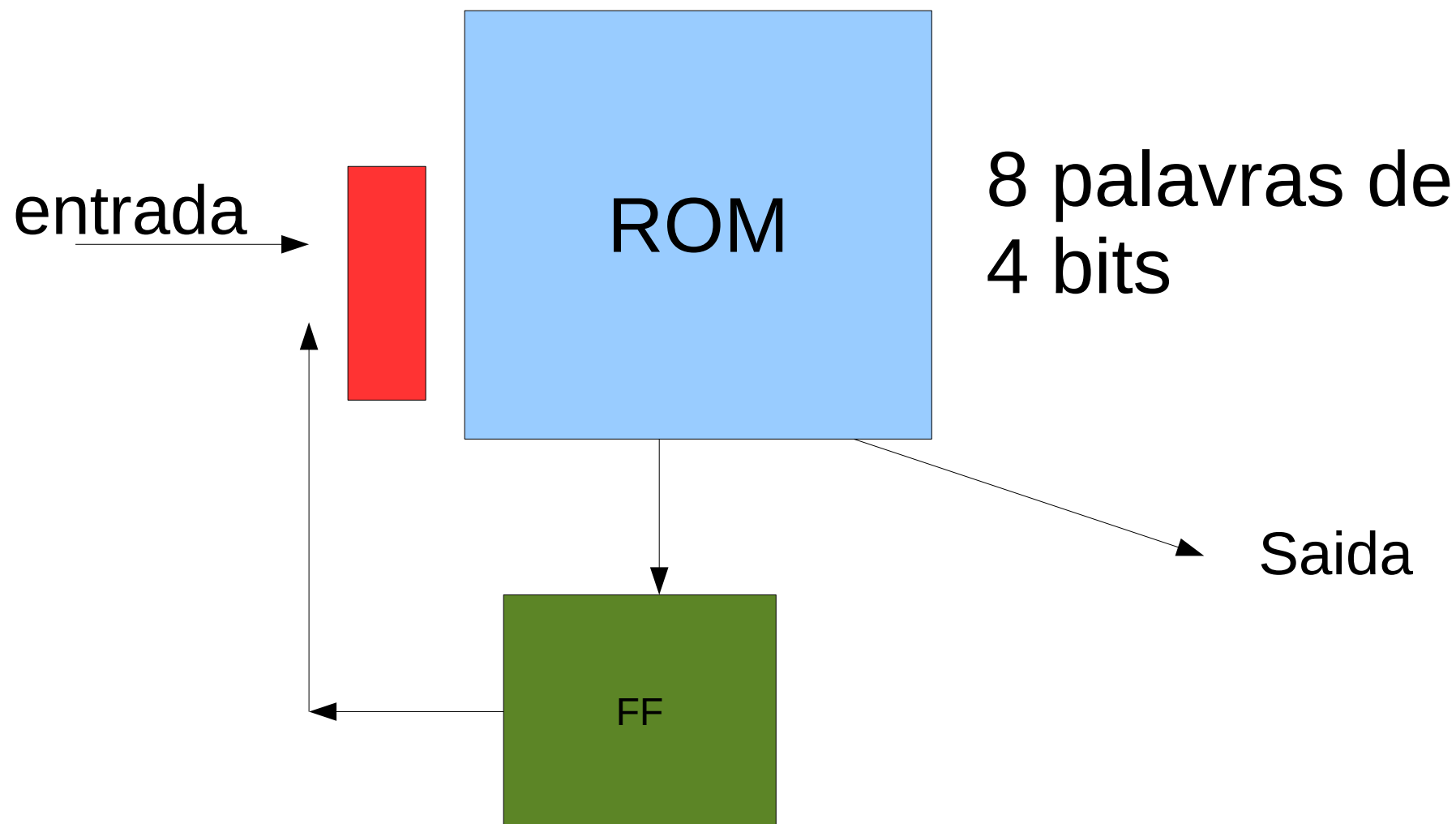

Ex4 teste 2011




A com 1 bit

A=0 fazer 0,2,1,3,0,2,1,3

A=1 fazer 0,1,0,1,.....

Ex4 teste 2011

 

A com 1 bit

A=0 fazer 0,2,1,3,0,2,1,3

A=1 fazer 0,1,0,1,.....